

# SYSTEMS I — LAB 7

## Designing an ISA and a CPU

This lab is really a final project—an assignment for which you will **work in pairs** for the remainder of the semester. It is an excellent way to develop and test your understanding of not only the assembly programming material that we have covered, but of the datapath and control material that we have covered. Therefore, it is essential that you invest real time and effort in this project. Not only is it critical for your understanding of the most central material of the course, but the grade from this lab will count far more than the other labs.

### 1 Designing your own ISA

The first stage of this project requires you to design your own *instruction set architecture (ISA)*: a specification for format of machine code words and their meaning. You must define the size of each machine code instruction, how its bits are divided, what the values for each of those bits imply, and how the flow from one instruction to the next should progress. There is nothing magical about any one design or another; each design decision involves a tradeoff. Specifically, an ISA that allows you a simpler CPU datapath and control may be more complex to program, or *vice versa*. Your primary goal is to **design something that works**. To the extent that you can choose your tradeoffs, you should try to do so.

Your ISA should be designed within the following constraints:

1. **Word length:** The machine word should be one byte (8 bits). That means that each register should hold one byte, and that each memory address should be one byte. Consequently, your main memory should  $2^8 = 256$  bytes long.
2. **Instruction length:** A machine code instruction may consist of as many words as you like. I strongly recommend that it be a fixed number—that is, don't try to vary the length of the instruction depending on the opcode, since that approach requires a more complex CPU control unit.
3. **Registers:** Your ISA must specify how many addressable registers are available for an instruction to use. You may even choose to have **no** registers, where your instructions use only main memory addresses.

Alternatively, you may assume a register file with as many registers as you like. I recommend choosing a power of 2 (thus avoiding the possibility of instructions that contain, in the bits that choose a register number, and invalid register address), and I also recommend not exceeding 8 registers (just to keep the task of constructing the CPU tractable).

4. **Capabilities:** Your ISA must be capable of the following operations:

- *Data movement:* A program must be able to load constants into either registers or main memory locations (or both); it must also be able to copy values between registers and/or main memory locations. You must provide instructions sufficient to set constants and move data. Note that you may choose to provide a minimal set of instructions, and

require the programmer to perform multiple steps for some kinds of data movement. For example, to move from one main memory location to another, you may require the programmer to copy a value from the source main memory location into a register, and then copy it from the register to the destination main memory location. Such requirements save you the work of also creating an instruction that is capable of directly copying data from one main memory location to another.

- *Logic*: Your ISA must allow for bitwise AND and OR operations on two input values, and NOT on a single input value. It may also provide other logic operations, such as XOR, NAND, NOR, etc.; however, keep in mind that if you provide the required operations, those are sufficient for performing any other logic operation in software.
- *Arithmetic*: There must be instructions to perform *addition* and *subtraction* on two input values, using two-complement to represent negative integers. You may optionally provide instructions for *multiplication* or *division*, as well as any other arithmetic operation that appeals to you.
- *Unconditional branching*: There must be at least one type of *jump* instruction. You may choose to use labels (i.e., immediate constants) as the jump targets. These constants may be expressed either as literal main memory locations or as offsets from the PC (depending on the size of your instructions). The jump target could also be register-based, where the branch target is taken from a register or main memory location. You can provide multiple *jump* variants, but you need only one. Note that you do **not** need a *call* instruction—procedure’s a useful constructs, but the complexity isn’t necessary for this assignment.
- *Conditional branching*: You must provide the ability to compare two values for equality or inequality, and the to branch only if that condition is true. How you structure these instructions is up to you. Note that you can rely on the programmer to perform some arithmetic first. For example, you may choose to provide only comparisons to zero (*equal to zero*, *less than zero* or *negative*, *greater than zero* or *positive*); with that ability to perform comparisons, any comparison between two values is possible when combined with simple arithmetic operations.

## 2 Designing a CPU to implement your ISA

Once you have specified your ISA, you must build a CPU to carry out instructions of that form. In particular, you must **build a full datapath and control**. Your design must include a register file (if your ISA assumes any addressable registers), a main memory, a PC, and an ALU. It should be possible to load the main memory with instructions of the format specified by your ISA, and then to have your CPU carry out the program specified by those instructions.

For this task, you will use `tkgate`, a circuit simulator. To use it, you need to login to `remus/romulus`, and then issue the command:

```
$ tkgate &
```

This simulator begins with a tutorial on its use. You can also visit the `tkgate` web site to find more documentation. Section 4 of this lab describes some additional features of the simulator that are useful but not (well) documented.

Note that the simulator contains pre-made ALU, main memory, and register modules that should make your task simpler. However, there are many details for which you must design and connect to your datapath and control. Expect that creating the CPU in the simulator will take some time.

## 2.1 Design decisions

The description above leaves a great deal of design space within which to work. Moreover, many of the choices that you make in designing your ISA will influence and constrain the datapath and control that you build to implement that ISA. You may find that once you consider these constraints—that is, once you see how your datapath and control would need to be constructed—you may choose instead to modify your ISA in order to simplify your hardware implementation.

**Instruction length:** Multiple-word instructions can make the programming task easier, but that choice implies that your CPU will require multiple clock cycles to carry out each instruction. For each word of the  $n$ -word machine code instruction, at least  $n - 1$  cycles will be required to load the first  $n - 1$  words of the current instruction into temporary registers. At the earliest, on the  $n^{\text{th}}$  cycle the processor will have all of the bits of the instruction available to decode and execute. Thus, your control unit's inputs are no longer just the opcode, but also the cycle number for the processing of this instruction.

**Unaddressable registers:** Perhaps a single-word instruction would be better? Yes, single-word instructions can be loaded from main memory and then immediately decoded and executed, avoiding the need (at least in terms of fetching the instruction) for multiple clock cycles per instruction. However, you may have noticed that a single word may have insufficient space to specify all of the registers, addresses, or immediate values that you desire. For example, if you want to add the values from two registers and store the resulting sum in a third register, there simply are not enough bits in one word for an opcode and three register numbers.

What to do? Create instructions that **perform simpler tasks** and that store those results in an intermediate register called an *accumulator*. So, for example, consider that to add the values in two source registers and then store the sum in a third register, you split the task across multiple instructions. One possibility is that you specify an `add` on the two source registers, but you don't specify a destination register. The result of the addition is placed into the accumulator so that the next instruction can `copy` the contents of the accumulator into the destination register. The programming task becomes more difficult, but the circuit design may be simpler.

**Main memory access:** Each main memory address is a one-word value that specifies a particular byte in the main memory. However, depending on how you have structured your ISA and imagined your CPU datapath and control, you may have to think carefully about how main memory is used.

For example, consider the an instruction that copies a value from main memory and into a register. To perform this task, the instruction itself must be loaded from main memory, and then the

value requested must be read from main memory as well. Since the main memory must be read twice for a single instruction, a multi-cycle control is necessary.

Another approach is to divide main memory into two components. The first component can be used to store only instructions, and the machine code of any program would have to be placed here. The second component can contain only data, and be accessed only by *load* and *store* instructions. This approach is less realistic than a real CPU using a typically unified main memory, but it is a reasonable approach to creating a working CPU.

This list of design issues is hardly comprehensive, but it includes a few of those likely to affect your ISA and CPU designs. Thinking ahead about them may help you to save time, and to see the breadth of possibilities.

## 3 Testing your CPU

In order to determine whether your datapath and control work properly, you'll need to test it. Initially, you should hard-wire certain input patterns to your datapath to be sure that smaller components are responding properly. Once that's done, you need to write small programs to test the CPU's function overall. You should begin with extremely simple programs (e.g., add two numbers). Then move onto something slightly more complex (e.g., a simple loop).

### 3.1 Assembling

You should write your programs in assembly. However, you then need to assemble these programs into machine code instructions. You can either perform this translation by hand, or, if your programming skills allow it, write a simple program to perform the translation for you. If you're feeling adventurous, you could even implement a few pseudo-instructions to make the higher-level, assembly programming task easier. Doing so is not at all required, though.

### 3.2 Loading and executing

You must be able to load a sequence of machine code instructions into your main memory for execution by the CPU. Assuming that you load your instructions into main memory address zero, you need only then to set your PC to 0, and then let the CPU fetch, decode, and execute each instruction in turn.

## 4 Poorly documented aspects of `tkgate`

The `tkgate` program, while quite useful, is not as clearly and thoroughly documented as one might like. Below are descriptions of two of the thornier problems of using this circuit simulator. In particular, for both of these, we walk through the construction of examples that should sufficiently illustrate how to perform these tasks.

## 4.1 Module inputs and outputs

When creating a module, the `tkgate` tutorial shows you how to create input and output *ports*. However, it does not show you how properly to connect those ports to actual gates. Follow this sequence to see how to create a simple module where the ports are properly connected and function:

1. Run `tkgate`.
2. From the **File** menu, select **New**. Click **OK** to create the file `new.v`.
3. From the **Module** menu, select **New...** Name the new module something not so clever, such as `notit`, and click **OK**.
4. On the left-hand side of the window, there is a list with the heading **Modules**. Double-click on `notit`. At the bottom of the window, you should see: `File: new.v Module: notit`.
5. From the **Module** menu, select **Edit Interfaces...** That will bring up a box, labeled `notit`, that represents your module.
6. On the left-hand side of that box, right-click to obtain a drop-down menu, and select **Add Input...** When the **Port Parameters** window appears, set the **Signal Name** and the **Port Name** both to be `a`. Click **OK**. You should see the box again, now with the label `a` and an arrow pointing into the box.
7. Similarly, on the right-hand side of the box, right-click and select **Add Output...** Set the **Signal Name** and the **Port Name** both to be `y`, and then click **OK**. You should see the box with the added label `y` above a little arrow pointing out of the box.
8. Once again go to the **Modules** list and double-click `notit`. You should now see, on the lower left-hand side of the window, the list **Ports** with `< a` and `> y`.
9. In the middle of the window, left-click somewhere. Then, from the **Make** menu, select the **Gate** submenu, and then select **Inverter**. A NOT gate should appear.
10. Somewhere to the left of the NOT gate, left-click again. Then, from the **Make** menu, select the **Module** submenu followed by **Module Input**. In the **Net Parameters** window that appears, set the **Net Name** to `a`. Click **OK**.
11. Use the *Move/Connect* tool to solder the wire coming from `a` to the input of the NOT gate.
12. Somewhere to the right of the NOT gate, left-click one more time. Then, from the **MAKE** menu, select **MODULE** and then **MODULE OUTPUT**. In the **Net Parameters** window, set **Net Name** to `y` and click **OK**.
13. Solder the wire from the output of the NOT gate to the output wire `y`.
14. Under the **Modules** menu, double click on `main+`, bringing you back to the main design space.

15. Left-click somewhere in the design space. Then select **Make** → **Modules** → **Module Instance**. When the **Gate Parameters** window appears, set the **Function** to be `notit`. Click **OK**. You should see a `notit` box appear with the *a* and *y* ports.
16. To the left of the module, left-click somewhere. Then select **Make** → **I/O** → **Switch**. Solder the switch to the *a* input of the module.
17. To the right of the module, left-click somewhere. Select **Make** → **I/O** → **LED**. Solder the *y* output of the module to this LED.

That's it. You've defined a module (`notit`) and connected external inputs and outputs to an instance of it. To test it, select **Simulate** → **Begin** and then **Simulate** → **Run**. You can then click the switch to toggle its value, and the LED will always show the opposite value, demonstrating that the NOT gate inside the `notit` module works.

## 4.2 Pre-loading RAM and ROM contents

The `tkgate` simulator allows you to add RAM and ROM modules to your circuits. By default, these memory components take an 8-bit address and store 8-bits per entry, which is perfect for this assignment. The trick is to pre-load these memory modules with values from some pre-written file. To see how you can make such a memory module, pre-load its contents, and then use it, follow these steps:

1. In `emacs`, open a new file and name it, say, `test.mem`.
2. Type, as text and in the following format, a few values to be loaded into the memory:

```
0/ 00 02 04 06 08 0a 0c 0e
8/ ff ee dd cc bb aa 99 88
```

In this format, the number preceding the slash is the address (in hexadecimal) at which the next group of values should be loaded. In the example above, the values will be loaded starting at address 0. The values that follow the slash are pairs of hexadecimal digits, where each pair represents a 1-byte value. Here, I chose meaningless but distinct values that should make it easy to determine that the memory module loaded the values correctly.

3. Open `tkgate` and create a new file.
4. Left-click in the design space. Select **Make** → **Memory** → **ROM**.
5. Double-click on the ROM module and a **Gate Parameters** window will appear. Click the **Details** tab, and then the **Browse...** button. Navigate your way to your `test.mem` file and select it. Click **OK**.
6. To the left of the ROM, create a **DIP Switch**. Solder its output to the *A* input of the ROM.
7. To the right of the ROM, create a **7-Seg. LED (Hex)**. Solder the *D* output of the ROM to the input of that LED.

8. Below the ROM, create a Ground and solder it to the  $\overline{OE}$  input.

To test this structure, start the simulator and run the simulation. You can double-click on the DIP switch to enter a new value (in hexadecimal) that will be presented as an address to the ROM. Given the example file above, only addresses 0 through  $f$  will produce an output. You should see, for each address, the corresponding two-digit hexadecimal value from the value corresponding to that location.

## 5 How to submit your work

Use the `cs16-submit` command to turn in your design. Note that only one member from each pair needs to perform this submission, and that you should label your work, clearly with text, the names of **both** members of the pair. Submit your circuit design and memory files. For example:

```
cs16-submit lab-7 cpu.v test-program-1.mem test-program-2.mem
```

**This assignment is due at 5:00 pm on Tuesday, December 22.**