

# SYSTEMS I

## LAB 2

### A 4-bit incrementor

**This assignment is due Thursday, Feb-12, 11:59 pm.**

For this week, we will perform a slightly different kind of arithmetic operation—similar to the addition we have discussed during lectures, but a bit specialized and thus simplified. This one will later be used, in Lab 3, to build a fundamentally different kind of circuit.

## 1 The project: an *incrementor*

You will design and implement a *4-bit binary incrementor*. There are 16 possible integers that can be formed with 4 bits, from 0 to 15 (or, in binary, from 0000 to 1111). Given that the incrementor should add 1 to each of these possible input values, we can make a table that shows each possible input value and its corresponding output value:

(original) input value	(incremented) output value
0	1
1	2
2	3
3	4
4	5
5	6
6	7
7	8
8	9
9	10
10	11
11	12
12	13
13	14
14	15
15	0

Notice that when the input is at its maximum possible value (15), the output “wraps around” to the minimum possible value (0).

## 2 A suggested approach

Here is a set of suggested steps that may help you both solve this problem and implement your solution as a circuit:

1. **Determine the output functions:** The output of your circuit should be a 4-bit number. Therefore, you have four output bits, each of whose value is determined by some Boolean logic function composed of the four inputs. Write out a truth table for the four input bits and their corresponding output bits, and then use the table to write the four output functions in disjunctive normal form.
2. **Simplify the output functions:** The output functions determined in the previous step are helpful, but likely more complex than necessary. Use Boolean algebraic transformations to simplify those functions.
3. **Draw the circuit:** Draw a circuit that computes the four simplified output functions that you developed in the previous step. You may have to draw the circuit a few times to come up with a clean layout that is easy to read.
4. **Build the circuit:** Use the switches, LEDs, chips, and wires to implement the circuit you've drawn. Be sure to leave time for debugging!

## 3 Submitting your work

**What to submit:** For this lab, you must submit:

1. **Your logic and circuit diagram:** As a PDF (which can be a scan if it is written on paper), show your *truth table*, *logic expressions*, and *circuit diagram*.
2. **Your working circuit:** A video of your incrementor on *all sixteen possible input patterns*. Move through the inputs in order, clearly showing the setting of the input switches and the outputs shown on the LED's for each possible input combination.

**How to submit it:** I have created and shared with each of you a Google Drive folder for this course. Within that folder, you should find a `lab-2` subfolder. **Upload your PDF and video into this folder** to submit your work.